

# National University of Computer and Emerging Sciences, Lahore Campus



Course:	Computer Architecture	Course Code:	EE204
Program:	BS(Computer Science)	Semester:	Fall 2017
Due Date:	11-09-2017	Total Marks:	80
Section:	A, B,C	Weight	3.3
	Assignment 1	Page(s):	2

**Note: Submit hard copy of the assignment before 5pm.**

**Q1:**

a) Using Boolean algebra proves that the following two functions are equal. (10 marks)

$$F(X, Y, Z) = \overline{(\overline{X})(\overline{Z}) + Z + Z(\overline{Y})} + (X + 0)(\overline{Z} + Y)(\overline{Z} + \overline{Y})(Y + 1)$$

$$G(X, Y, Z) = X(\overline{Z})$$

b) Represent the decimal number -18.625 into IEEE 754 binary representation

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0

**Q2: Represent the following two numbers in normalized form using scientific notation (10 marks)**

**A = 1011 1110 1110 0000 0000 0000 0000 0000**

**B = 0100 0110 1101 1000 0000 0000 0000 0000**

and then perform following operations showing all work

- a.  $A - B$
- b.  $A * B$

**Q3: Design a 3-bit binary counter and shifter with parallel load and synchronous clear. (Arithmetic shifts are required)**

**Make Function table and draw the circuit diagram. (15 marks)**

**Q4:  $A = (13)_{10}$   $B = (6)_{10}$**

**Use all three multiplier circuits studied in this course to compute  $A * B$ . Show the binary values of all the registers at every time step. (15 marks)**

**Q5: Draw a sequential circuit that has two D flip-flops, A and B, maintaining state, two inputs X and Y and one output Z. The output and next flip-flop states are given by the equations.**

**(15 marks)**

$$\begin{aligned}A_{i+1} &= \bar{X}Y + XA_i \\B_{i+1} &= X\bar{B}_i + X\bar{A}_i \\Z &= A_i(\bar{X}B_i + Y)\end{aligned}$$

- a) Draw the logic diagram of the circuit.
- b) Tabulate the state table
- c) Draw state diagram

**Q6: Design a 4-bit ALU that supports the following operations:**

**(15 marks)**

- 1)  $A + B$
- 2)  $A - B$  (2's complement subtraction)
- 3) 1-bit right shift (apply to input A)
- 4) 2-bit right shift (apply to input B)
- 5) 1-bit left shift (apply to input A)
- 6) 2-bit left shift (apply to input B)
- 7)  $A \& B$  (bitwise AND)
- 8)  $A | B$  (bitwise OR)